

Lecture/Laboratory #13

- Lab Review
 - Lecture Review
-


- D/A and A/D converters
- Converter Errors
- Timing with Counters
- Latches and Registers
- Start of Digital Sampling Oscilloscope (Front end)

Lab ⇒ Connect A/DC with D/AC

Analog signal input → look for analog signal output (for restoration of analog signal accuracy)

Connect output of A/DC to LED and observe flashing

Digital – to – Analog Conversion

 

16 possible current (voltage) values depending upon which switches are closed.

$$R = 1 \text{ k} \rightarrow 2^0 (= 1)$$

$$R = \frac{1}{4} \text{ k} \rightarrow 2^2 (= 4)$$

$$R = \frac{1}{2} \text{ k} \rightarrow 2^1 (= 2)$$

$$R = \frac{1}{8} \text{ k} \rightarrow 2^3 (= 8)$$

Op-amp for voltage output.

For 12 – bit system range of resistor values 2000:1! Other solutions, which may not require such large range of resistors with precision determined by the smallest one.

Analog – to – Digital Conversion

A/DCs are available commercially as ICs (chips)

Number of different A/D converters


Parallel – encoded (“flash”) A/DC

It is the fastest method of A/D conversion. The delay time from input to output = comparator + encoder delays.

Commercial : 16 to 1024 levels


(4 – bit to 10 – bit outputs).

 Input V_{in} is fed simultaneously to one input of N comparators. Other inputs are connected to N equally space refer. Voltages. Encoder generates a digital output ~ to highest comparator by V_{in} .



A/DC – Successive Approximation

 Output codes (digital) are feed – in into D/AC and are compared with analog input via a comparator.





Start: all bits = 0 : MSB \Rightarrow 1 and following bits \Rightarrow 1. If D/AC output does not exceed the input voltage, this bit stays 1. Otherwise, it is set 0. For N – bit A/DC , N-such steps are required.
Successive approx. A/DC has begin conversion (“start”) input and conversion done (“end”) output. Digital output \Rightarrow parallel format.

Converter Errors


Errors related to A/D and D/A converters are in broad range. We will concentrate on the two most common types of converter errors.

Examples:

  

Timing with Counters

 Flip – flops and counters (cascaded toggling FFs) can be used to generate a long output pulse. IC 4060 is a 14 stage CMOS binary counter (14 cascaded FFs) \Rightarrow scheme and principle of work:



A rising edge at the input brings Q HIGH \rightarrow enabling counter.

After 2^{n-1} clock pulses (n_{\max} for our example is 14) Q_n goes HIGH resetting FF (4013) and the counter, and cycle can start again.

\Rightarrow Generation accurate long pulse, which length can be varied by 2 (depending on number of Q_n involved).

The 4060 has internal oscillator, which can eliminate need for external clock.


Latches and Registers

Latches and registers → to hold a set of bits even if inputs change.

Register: is a set of FFs

Latch: is a special register ⇒ outputs follow inputs when enabled, and hold the last value when disabled.

74 LS 174 is 4 – bit D register:

 


This is quad D register with true (Q) and complemented (\bar{Q}) outputs.


Latches and registers are available with three – state outputs (e.g. 4 – bit 8551 D – register), which can be used in data “bus”.

Digital Sampling Oscilloscope (DSO)

Block diagram:

 


Modes of Operation

 

1. Acquisition Mode (Memory) → Not fast
2. Display Mode (Reading from memory) → Fast
3. Transfer Mode ← Slow

DSO (cont.) Front End (cont.)

 

- (A) High Z_{input} Voltage follower:
 $Z_{in} = 2 \text{ M}\Omega$, $Z_{out} = 75 \text{ M}\Omega$
- (B) Variable gain amplifier: $Z_{in} = 10 \text{ k}$, Gain = 0 – 10 x
- (C) DC offset adjustment : $I_{in} \pm 2 \text{ mA}$ (adding voltage follower → better circuit)
- (D) Summing amplifier: Output here is DC adjusted
- (E) Sample – and – hold: $C = 0.01 \mu\text{F}$ was selected in order to provide sampling rate at 40 μsec with precision 1:256
 $\Rightarrow 40 \mu\text{sec} \times 256 = 10^{-2} \text{ sec}$
 $\tau = RC = 0.01 \mu\text{F} \times 1 \text{ M}\Omega = 10^{-2} \text{ sec}$

Start of Digital Sampling Oscilloscope (DSO)

Specifications:

Inputs: 1 channel (2 channels → by alternating →
(analog) → using 4066)

~ $10^6 \Omega$ impedance

- 5 → + 5 voltage range

0.5 – 20 adjustable gain

-5 → +5 adjustable bias

Outputs

(analog): ~ 100Ω output impedance

(digital): 1200 bane (= bit/sec) data transfer rate

Sampling and Memory:

~ 100 → 3 kHz adjustable sample rate

~ 2000 bytes RAM (Random Access Memory)
capacity

DSO (cont.)

Manual (Report)

→ Display (set up of the board, features)

Table of Contents

→ Introduction

- Specifications, General Description

→ Operation I (manual)

- PSs

- Channels (range)

- Offset and Gain

→ Operation II (details, “theory”)

→ Conclusions, Improvement Suggestions etc.

→ Figures (Figures can be both inside the text and at the end)

→ Tables

→ Appendix (A, B, C, . . .etc.)