

## Lecture/Lab # 17 & 18

- Lab Review
  - Lecture Review
- 


- Memory (ROM)
- Elements of Digital Sampling Oscilloscope – Connections
  - Front – End (see lecture #8)
  - A/D Converter
  - Tri-State Bus  $\Rightarrow$  A/DC, D/AC, RAM (ROM), UART and Computer connections
- **Discussion of Construction of Digital Sampling Oscilloscope (DSO)** (see also lecture #13)

# Discussion of Elements of Digital Sampling Oscilloscope (DSO)

Front – End → see Lecture 8

Important to use appropriate sampling rate  $\Rightarrow$  clock (which may be one for all system) rate has to be properly divided to fit to S/H rate

## A/C Converter

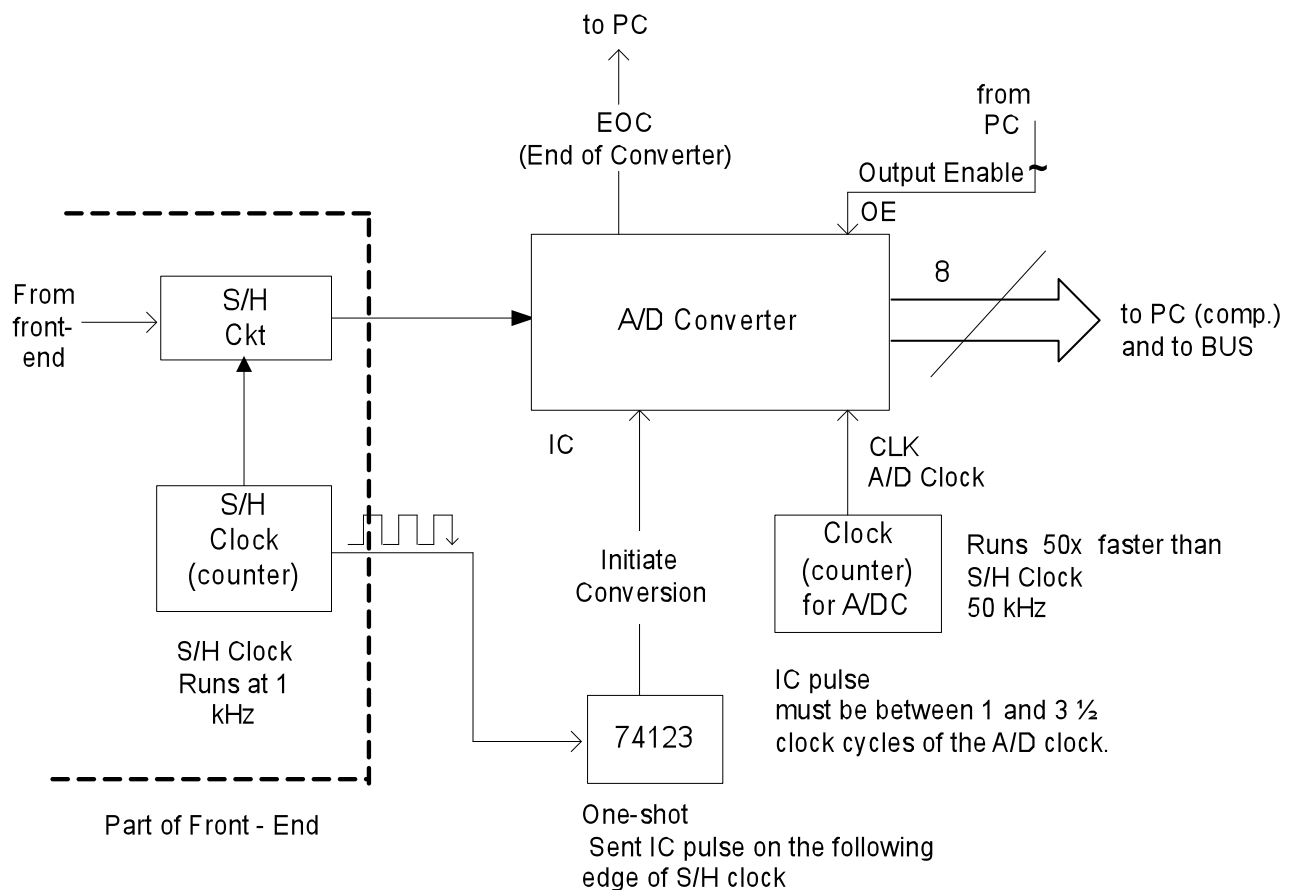

## DSO (cont.)

### A/D Conv. (cont.)

The analog signal from the output of front – end (S/H circuit) goes to A/D converter.

A/DC will convert analog signal into 8-bit digital word. The word will be sent from the A/DC through the controlling microprocessor to the data latch and into the RAM.


It requires 40 clock cycles to get converted signal in A/DC -800 ( 804 requires >70 clock cycles) by successive approximations.

### Tri – state Bus

The A/DC, D/AC, Data Latch, RAM (ROM), and PC computer will be connected to the Tri-state bus (under control of the computer) that will master sequence of the acquisition and transmission of data throughout the process

## DSO (cont.)

### Tri – state Bus

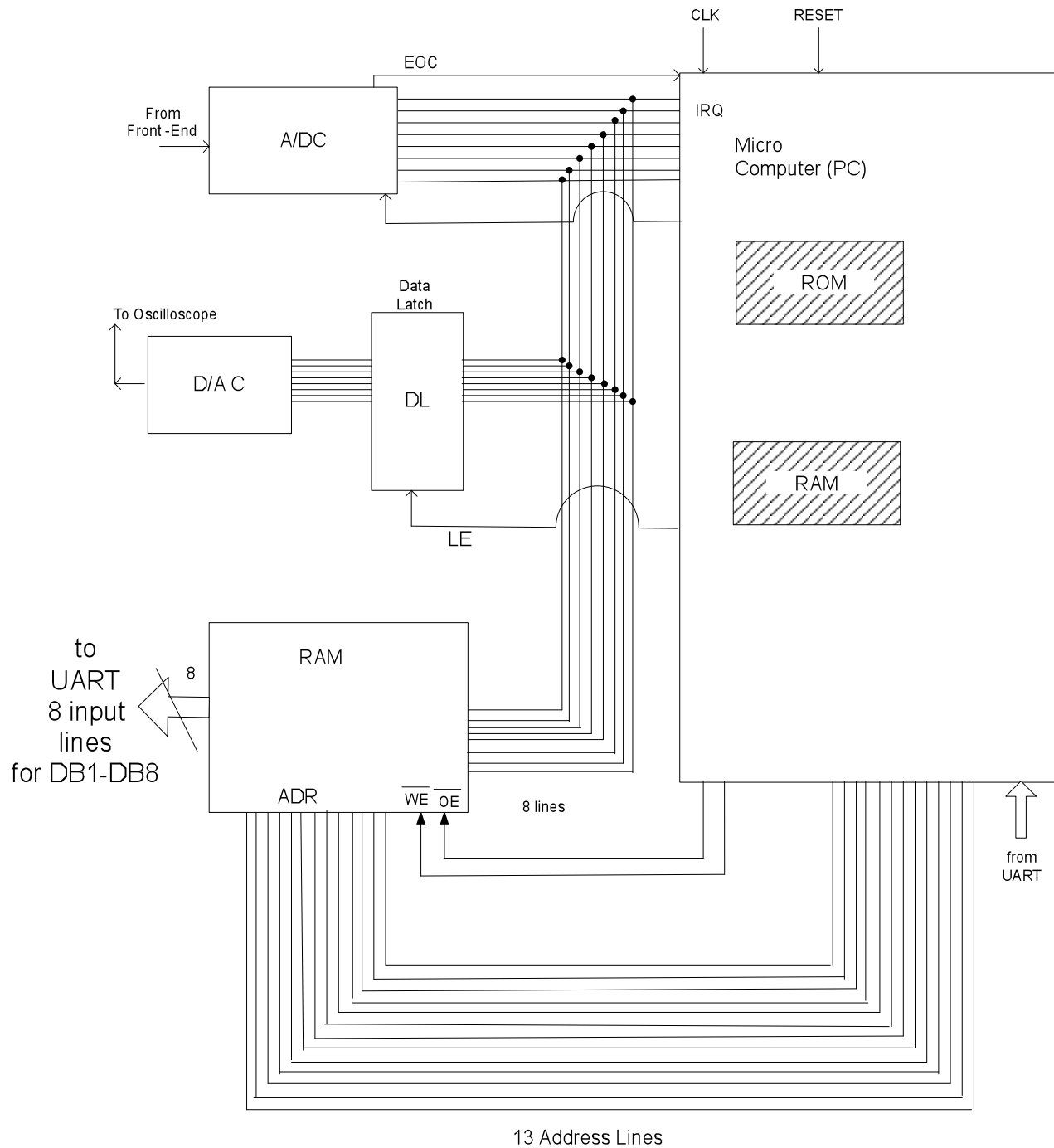

# Discussion of Construction of Digital Sampling Oscilloscope (DSO)

Remembering about manual coverage of:

- features (also location of elements on board)
- table of contents
- specifications (e.g. data sampling rates)
- principle of operation and function of major elements

---

Different schemes possible (equivalent) (see examples)



---

Principle of design and construction

- calculation of clock rates for different parts of DSO
- compactness

# Digital Sampling Oscilloscope (DSO)

## Block diagram:

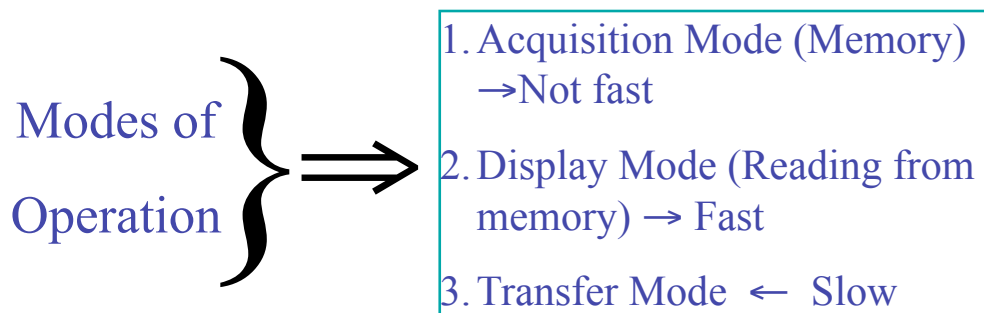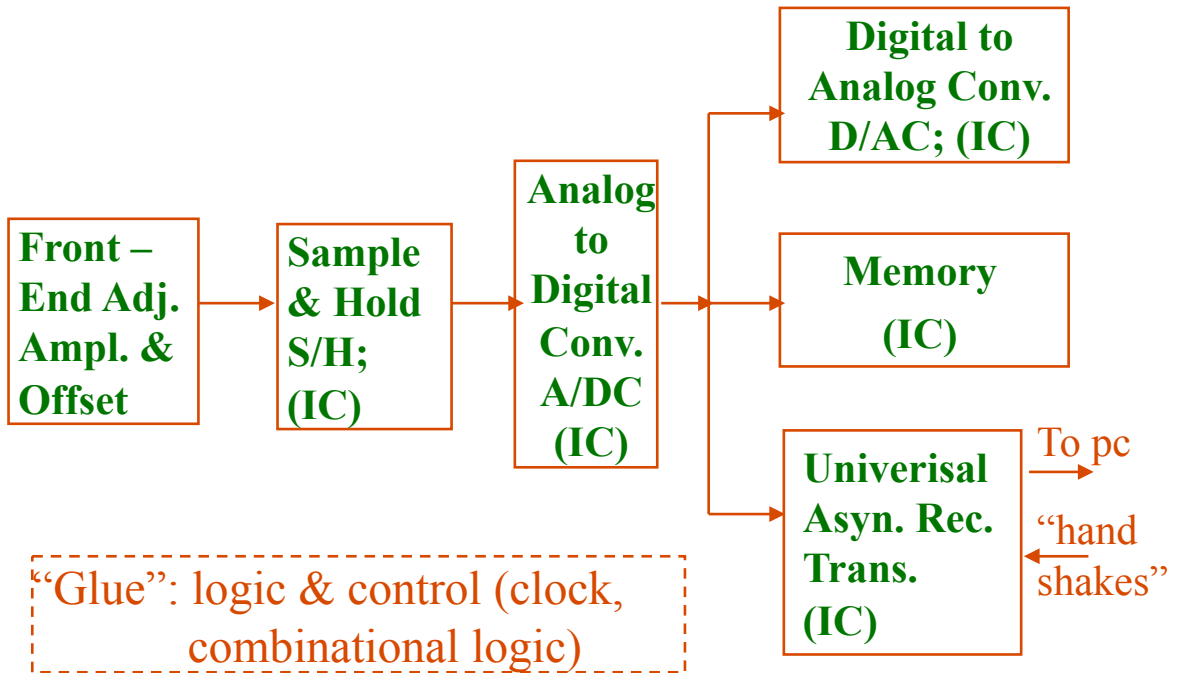

## DSO construction (cont.)

Attention to:

- Possibility to view digitized signal directly (not stored)  
⇒ digitized signal to D/AC and from D/AC to oscilloscope
- Playing back data from memory
- Calibration ⇒ known voltage on input → adjustment of gain and offset until output voltage = input voltage.

## Analysis of one of the schemes

Input signal processing:

From unity gain op-amp signal goes to analog switch (4066), which switches the signal between two S/Hs → one is sampling, another is holding (avoid limitations for capacitor charging)

## DSO construction (cont.)

### Analysis of one of the schemes (cont.)

The outputs from S/Hs go to another set of analog switches (the same 4066), which combine two S/Hs signals  $\Rightarrow$  signal goes to another op-amp, which is also buffer between front-end and A/DC.

Bit rate generator MC 14411 provides clocking for 4066.

#### Conversion:

A/DC  $\Rightarrow$  ADC 0800. Clock for A/DC  $\rightarrow$  from MC 14411. Minimize noise in ADC 0800 (wiring) and eliminate spikes (use capacitors for HF filtering: e.g. 4.7  $\mu$ F capacitor).

Zero and full scale calibration for A/DC  $\Rightarrow$  “0” – by adding resistor (e.g. 680  $\Omega$ ) to pin 5; 11111111 to 11111110 transition for 0.5 LSB voltage ( $\sim 20$  mV for 10 V input scale).

Full Scale – resistor to pin 15 (e.g. 1.5 k $\Omega$ );

00000001  $\rightarrow$  00000000 transition for 1.5 LSB  
from full scale



## DSO construction (cont.)

MC 14411  $\rightarrow$  1.84 MHz crystal  $\rightarrow$  614.4 kHz clock  $\rightarrow$  A/DC is clocked at 614.4 kHz and at 12.8 kHz or 9.6 kHz conversion clock (48 or 64 cycles, respectively for single conversion; 2 – 4 cycles for initiation conversion  $\rightarrow$  between conversion).

Buffering by using inverted gates.

Conversion start by one – shot made of two FFs (can be done e.g. with timers or counters).

Conversion clock (12.8 or 9.6 kHz) is divided by 2 in another D – FF and it is used to switch 4066 for driving two S/Hs (  $Q$  and  $\overline{Q}$  from D – FF). Conversion has to start after S/H switching (with appropriate delay in order to avoid interference with switching).

Signal to and from the RAM:

RAM with adjustable storage rate (instead of adjustable a/DC sampling rate)  $\Rightarrow$  low frequency signal can be stored in the limited memory without filling it too quickly.

## DSO construction (cont.)

Variable storage rate  $\Rightarrow$  RAM clock and address counters dividing by  $2^0, 2^1, 2^2, 2^3$ , etc. and using data selectors to choose the desired rate of operation of RAM.

End of Conversion (EOC) and Start Conversion (CVN) are two clocks from A/DC to divider/data selectors ('151) and to RAM.

EOC clock's rising edge is synchronized with the completion data conversion and EOC's falling edge – with rising edge of the next start conversion pulse. EOC clock leads SC by 8 cycles ( $13\mu\text{s}$ ) – guarantee stability of address in RAM during writing