

Lecture/Laboratory #10

- Review Lab
 - Review lecture #9
-

- SR Flip – Flop
 - Clocked FFs
 - Edge – Triggered FFs (D – FF)
 - JK – FF and T – FF
 - Divider by 2^n
 - Monostable Multivibrators (“one – shot”)
 - Oscillators and Timer Chip (555)
-

Lab : Build frequency divider by $\textcircled{2^n}$


Sequential Logic

Devices with Memory


FLIP – FLOP → memory cell

\bar{R} / \bar{S} FF ← Reset / set Flip - Flop


\bar{R}	\bar{S}	Q	\bar{Q}	
Inputs		Outputs		
1	0	1	0	} stable
0	1	0	1	
1	1	{ Quiescent (no change)		{ Not allowed
0	0			

 

Used as switch debouncer

 


or

 

Equivalent presentation of ckts FF has two stable states (“bistable”).
Which state it is in depends on past history (memory)


RS Flip – Flop as Switch Debouncer

Switch “bounce”:

 

cure
↙


Switch debouncer:

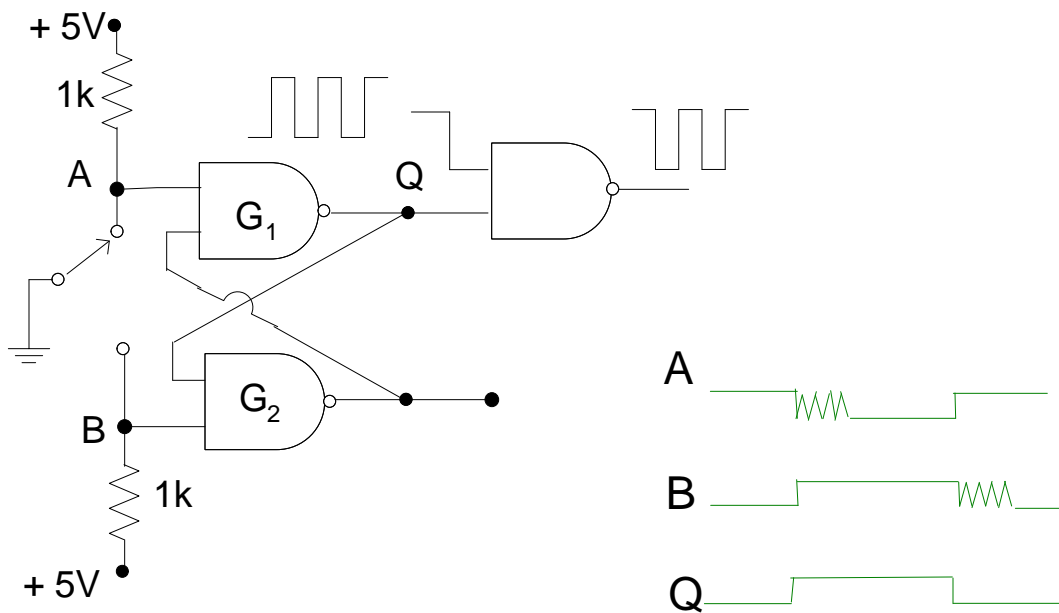

Clocked Flip - Flops

SR (set-reset) flip – flops can be forced into one state or the other by just putting the right input signal. They are useful for number of applications (e.g. switch debouncing). However, the most popular form of such flip – flops has a single “clock” input and one or two “data” inputs. The outputs can change state or stay the same \Rightarrow it depends on data during the clock pulse arrival.

The simplest clocked flip-flop:

 

Pair of gates controlled by clock
for SET and RESET inputs

Clocked Flip – Flops (cont.)

S	R	Q_{n+1}	
0	0	Q_n (no change)	Q_{n+1} is output (Q) <u>after</u> the clock pulse, and
0	1	0	
1	0	1	Q_n is output <u>before</u> clk pulse
1	1	Indeterminate (“no allowed” in previous)	

The main difference between this and previous SR flip-flop is that S & R now behave as data inputs. Output depends on value of S and R when clock pulse comes.


However, this flip-flop has one awkward property. Namely, the outputs can change during the time the clock is HIGH (1) if inputs change \Rightarrow similarly as regular SR flip-flop.

Such property can be avoided by using edge-triggered flip-flops (D-type flip-flops), often used in “master – slave” configurations.

Edge-Triggered Flip-Flops (-D Flip-Flops)

These are popular, inexpensive flip – flops, packed as IC. In these FFs the data on inputs just before a clock transition (“edge”) determines the output state after clock has changed.

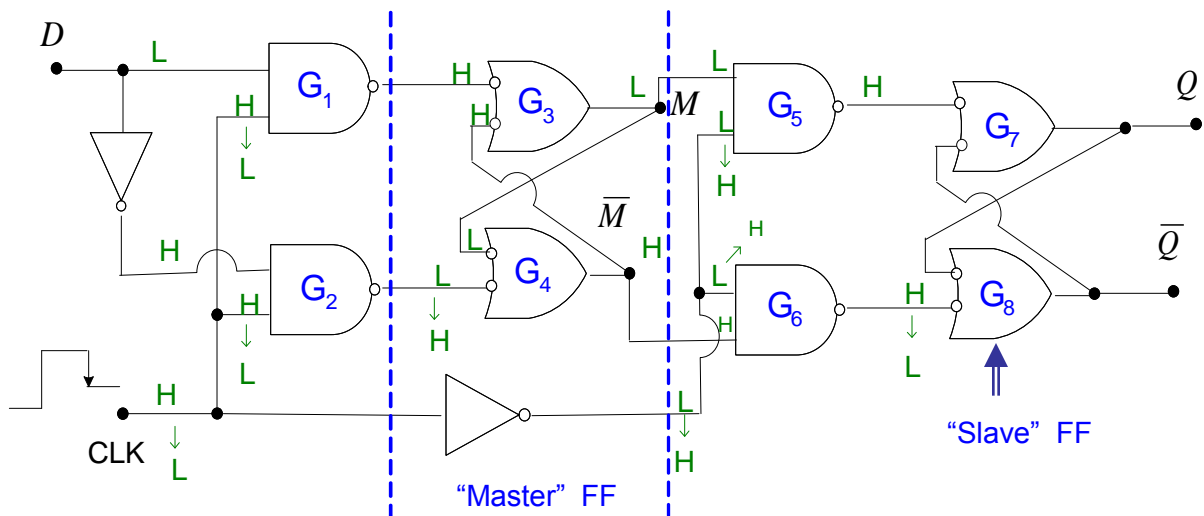Example of D – FF in “master-slave” configuration:



Analysis:

- (a) CLK HIGH \Rightarrow G₁ and G₂ are forcing “master” FF (G₃ and G₄) to the same state as input D $\Rightarrow M = D$ and $\bar{M} = \bar{D}$. Output from G₅ and G₆ is HIGH. If outputs from G₅ and G₆ are HIGH, then outputs from G₇ and G₈ will be the same as before (no change)


D Flip – Flops (cont.)

(b) CLK goes LOW \Rightarrow outputs from G_1 and G_2 are HIGH independent of input D.

\Rightarrow outputs from G_3 and G_4 are independent of D, therefore “master” FF outputs are transferred to “slave’s” inputs and no further changes can occur until next rising edge of the clock.

(c) At the next rising edge of the clock (CLK goes HIGH) gates G_5 and G_6 decouple the “slave” from the “master” and G_1 and G_2 connect “master” with inputs $\Rightarrow M = D$.

Schematically D – FF:

 

Negative-edge-triggered:

Q = D for E goes HIGH to LOW

Positive-edge-triggered:

Q = D for E goes LOW to HIGH

J - K Flip – Flops

J – K FF works similarly as D – FF, but it has two data inputs.

Truth Table:

$$J = \bar{K} \Rightarrow Q_{n+1} = J$$

at next clock edge


$$J = K = 0 \Rightarrow Q_{n+1} = Q_n$$

no change



J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	\bar{Q}_n

$J = K = 1 \Rightarrow$ output will reverse its state after each clock pulse
– output will “toggle”

Examples of D – FF and JK – FF:

 


D – type FF (positive edge triggered)

  



JK – type FF (“master” – “slave”) (negative edge triggered)

T Flip – Flop and Toggling

 JK FF will toggle for both inputs HIGH ($J = K = 1$), as we have discussed. Practical use can be for making circuit, which divides by 2:



  More common method of toggling is by using modification of D – FF, called T – FF:




In T- FF input D is connected with its own complemented output \bar{Q} .

Therefore at the time of the clock pulse $D = \bar{Q} \Rightarrow$ output at $\frac{1}{2}$ frequency of the clock input.

Divider by 2^n

 T-FFs can be used for creation divider by 2^n . Because one T-FF can provide divider by 2, therefore n T-FFs can \Rightarrow by 2^n by connecting output of each one to next clock input:



Timing diagram:

